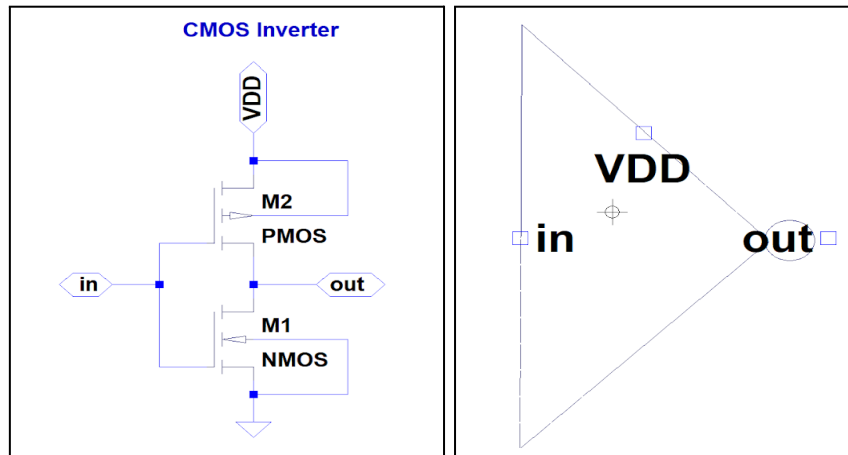



Inverter:

Circuit and Symbol:




The width(W) and length(L) of both PMOS and NMOS are $2\mu\text{m}$ and 130nm respectively.

Testbench:

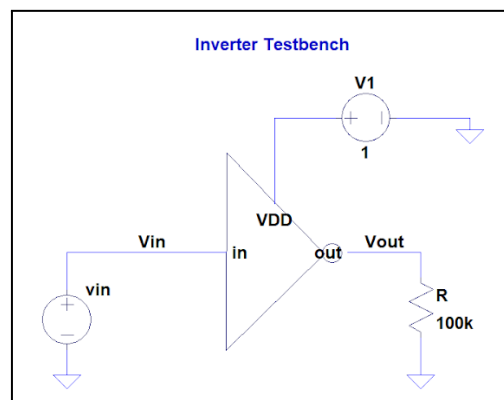

Transfer Characteristic:

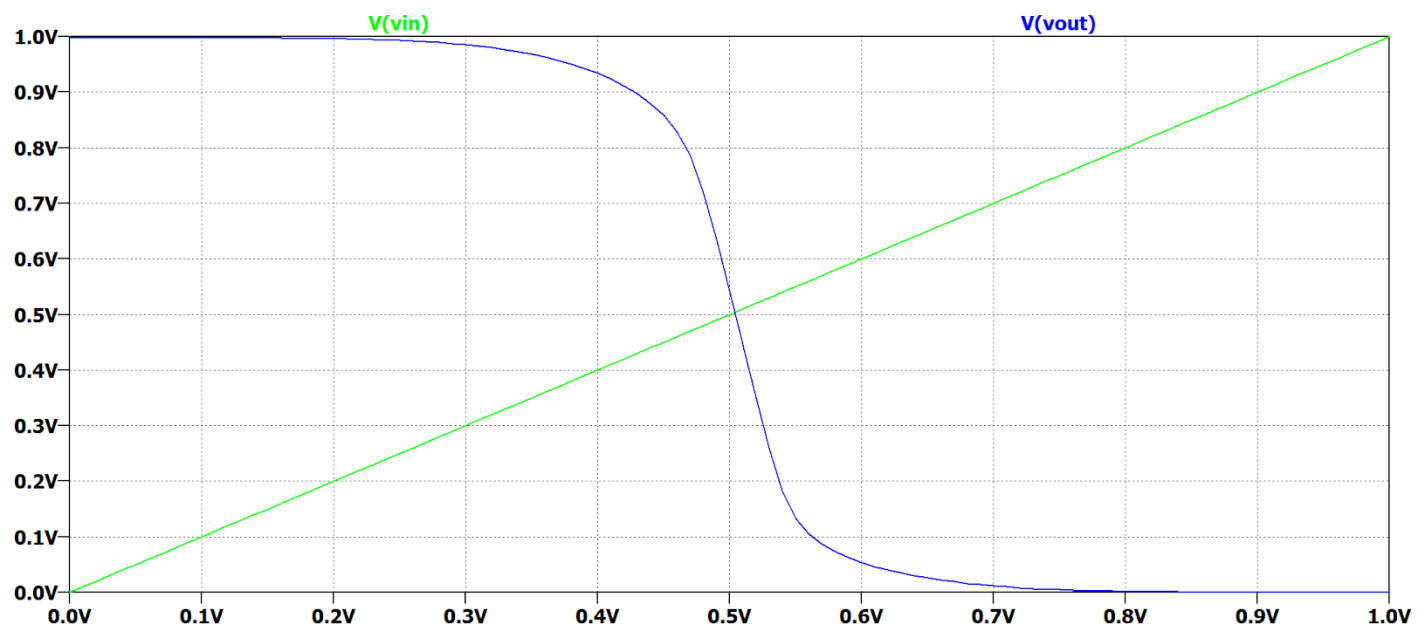

Transient Response:

